



Course Name:	Elements of Electrical and Electronics Engineering Laboratory	Semester:	✓ I/II
Date of Performance:	/ / 20--	Batch No:	C-5(3)
Student Name:	Sai Shivani maddala	Roll No:	60
Faculty Sign & Date:		Grade/Marks:	/ 20

Experiment No: 7

Title: Measurement of Power using Two Wattmeter Method


Aim and Objective of the Experiment:

- To measure the power of three phase power using Two Wattmeter Method

COs to be achieved:

CO2: Demonstrate and analyze steady state response of single phase and three phase circuits

Circuit Diagram:

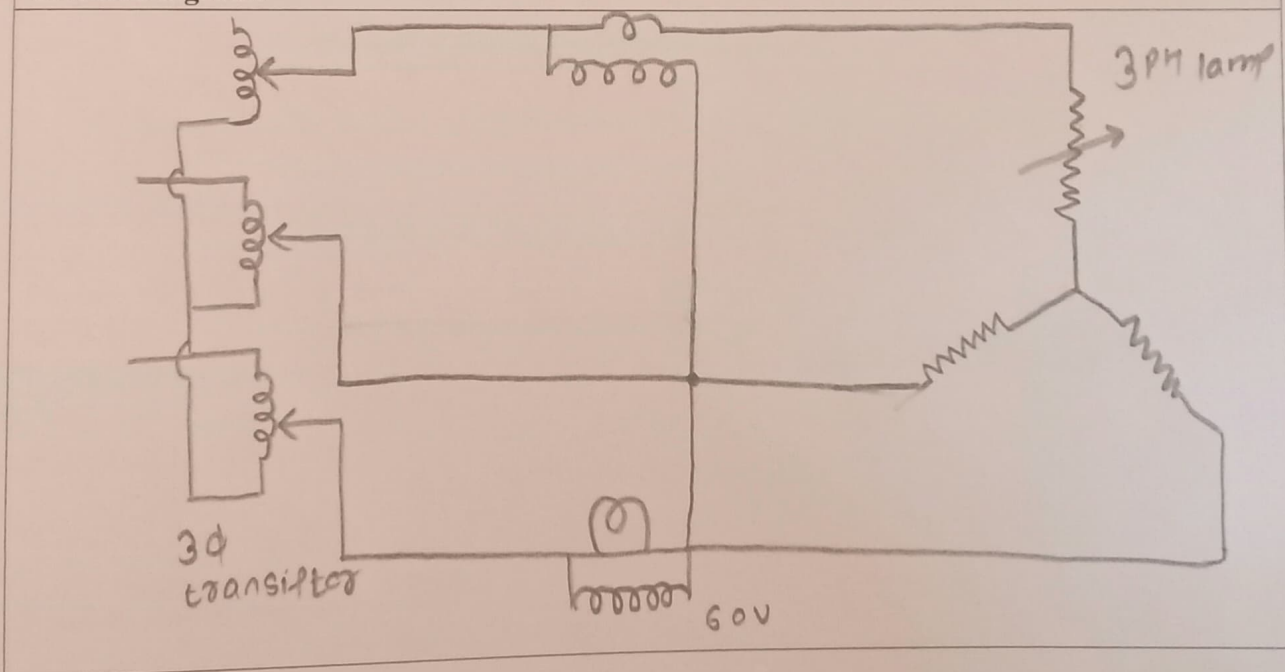

Stepwise-Procedure:

1. Connect the circuit as shown in circuit diagram
2. Increase the load and note down the reading V_L, I_L, W_1 and W_2
3. Practically you will obtain total power $W = W_1 + W_2$
4. Theoretically power is measured by using formula $P = \sqrt{3} V_L I_L \cos \phi$,
using $\cos \phi = 1$ (unity) for resistive load.

Observation Table:

Observation Table:

Sr.no	V_L (Volts)	I_L (Amp)		W_1 (KW)		W_2 (KW)		$W =$ ($W_1 + W_2$) (KW)		$P =$ $\sqrt{3} V_L I_L \cos \phi$ (KW)	Lamp load given from lamp bank (KW)
		TH	PR	TH	PR	TH	PR	TH	PR		
1	400	0.8	0.9	0.27	0.3	0.27	0.3	0.54	0.6	0.54	0.6
2	400	1.6	1.8	0.55	0.6	0.55	0.6	1.1	1.2	1.08	1.2
3	400	2.4	2.6	0.83	0.9	0.83	0.9	1.66	1.8	1.56	1.8
4	400	3.6	3.5	1.24	1.24	1.24	1.24	2.48	2.48	2.1	2.3

Theoretical Calculations:

$$\text{Power} = \sqrt{3} \times V_L \times I_L \times \cos \phi$$

$$\cos \phi = 1$$

$$\text{Power} = \text{Wattage rating of lamp load} \times \text{No of lamps (One lamp is of 100W rating)}$$

$$W_1 = V_L \times I_L \times \cos (30 + \phi)$$

$$\phi = 0$$

$$W_2 = V_L \times I_L \times \cos (30 - \phi)$$

$$\text{Total Power} = P = W_1 + W_2$$

Conclusion:

From the given experiment, the 2 wattmeter method proved to be an effective and accurate technique for measuring power in a 3 phase power system. The experiment successfully demonstrated the ability of the two wattmeter method to provide accurate readings of both active and reactive power in a balanced 3 phase system.

Signature of faculty in-charge with Date: